

CMPE2150 SA 06

SCR and TRIAC Circuits

Taylor, Moore, and Armstrong

10 Oct 2024

Table of contents

1. In an SCR circuit that uses a variable voltage divider from the AC supply waveform to trigger the Gate, the power can be controlled from:
 - ☐ 0° to 90°
 - ☐ 90° to 180°
 - ☐ 0° to 180°
 - ☐ 0° to 360°
2. Describe what would happen if the following circuit if the switch was closed and then opened.

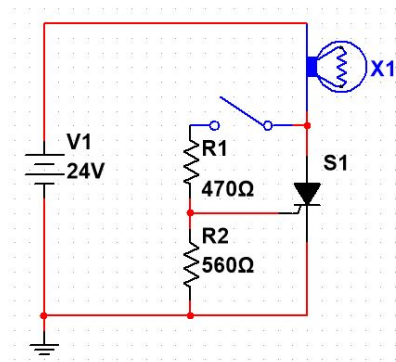


Figure 1: SCR Controlling a DC Source

- ☐ The lamp would start to glow, then stop glowing.
- ☐ The lamp would not glow.
- ☐ The lamp would start to glow and remain glowing.

3. Describe what would happen if the following circuit if the switch was closed and then opened.

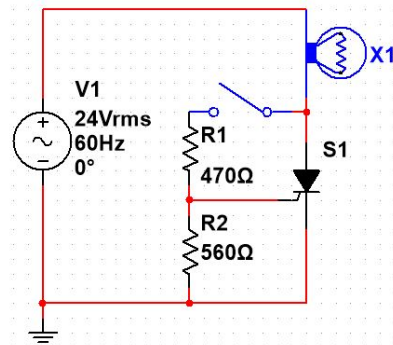


Figure 2: SCR Controlling an AC Source

- ☐ The lamp would start to glow, then stop glowing.
- ☐ The lamp would not glow.
- ☐ The lamp would start to glow and remain glowing.

Consider the following schematic when answering the questions below:

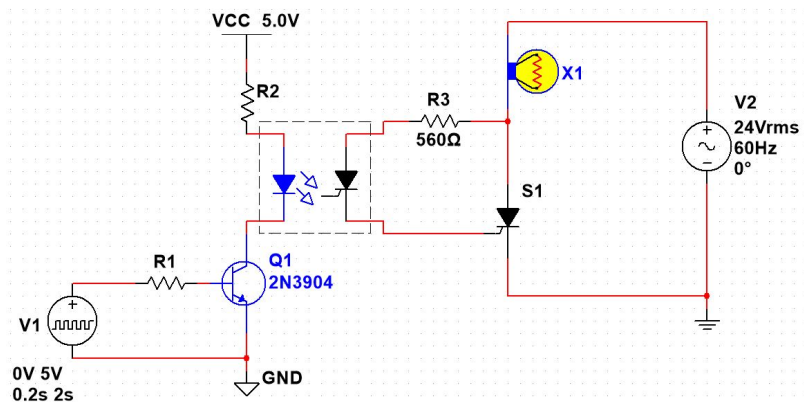


Figure 3: Optically Isolated SCR Circuit

4. If the LED in the optocoupler requires approximately $35mA$ to operate, pick a 10% standard resistor value for R_1 that would be about half the value calculated from the Active transistor model: _____ $k\Omega$ (this is identical to the rule-of-thumb we have been using for BJT saturation).
5. Also pick a suitable 10% standard resistor value for R_2 , given the conditions above: _____ Ω .
6. When the input signal is HIGH:
 - ☐ The lamp will glow with a continuous, full-power current.
 - ☐ The lamp will glow during each positive half-cycle.
 - ☐ The lamp will not glow.

7. When the signal is driven LOW after being HIGH:
- ☐ The lamp will continue to glow.
 - ☐ The lamp will not glow.
 - ☐ The lamp will glow at half-power.
8. This circuit could be made to control the brightness of the lamp if circuitry was added to detect when the AC power signal crossed zero volts once for each cycle. In this case, the frequency of the pulse would end up being _____ Hz . If the pulse was designed to drop to zero at the negative crossing point of the signal (i.e. when the sine wave changes from the positive half-cycle to the negative half-cycle), what duty cycle would turn the lamp off? _____ (0, 25, 50, or 100%) . What duty cycle would turn the lamp on at approximately half of the maximum power this circuit could provide? _____ (0, 25, 50, or 100%).
9. In a TRIAC circuit with a controller that doesn't incorporate a phase delay in its triggering circuitry,
- ☐ the power can be controlled from 0° to 90°
 - ☐ the power can be controlled from 90° to 180°
 - ☐ the power can be controlled from 90° to 180° and from 270° to 360°
 - ☐ the power can be controlled from 0° to 360°

For the following circuit:

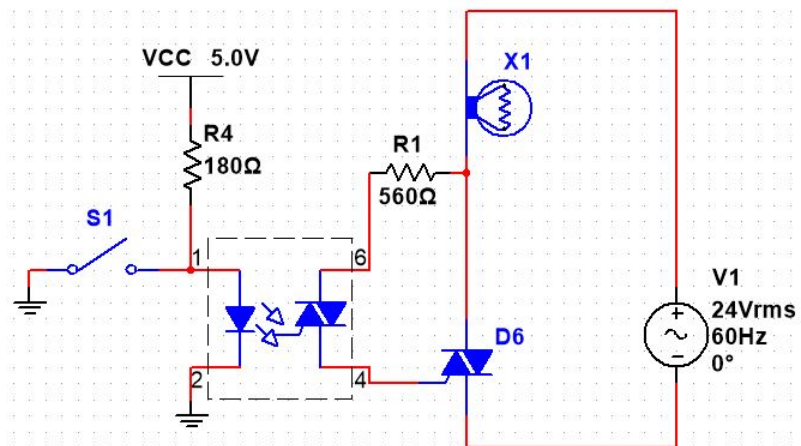


Figure 4: Optically Isolated TRIAC Circuit (AC Source)

10. If the switch is open, the lamp will _____ (glow/not glow).

11. If the switch is then closed, the lamp will _____
(glow/not glow).

For the following circuit:

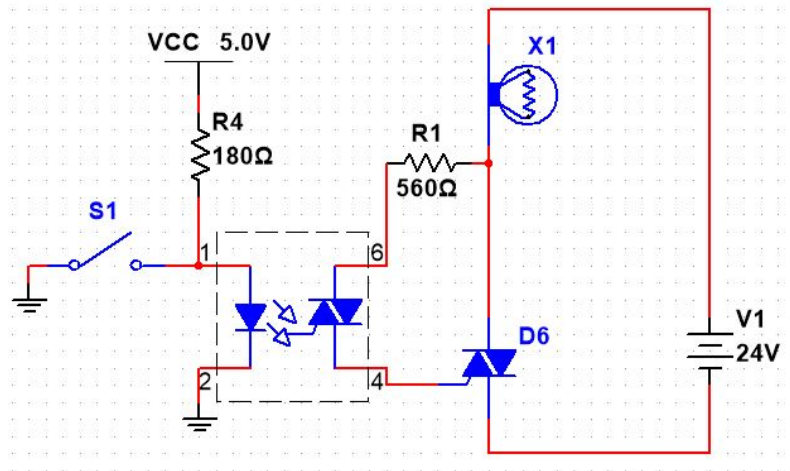


Figure 5: Optically Isolated TRIAC Circuit (DC Source)

12. If the switch is open, the lamp will _____ (glow/not glow).
13. If the switch is then closed, the lamp will _____
(glow/not glow).